

II PUC ELECTRONICS

Field effect transistors

1) A JFET has $g_m = 1500 \mu S$ and $r_d = 5 K\Omega$
Determine its μ

2) A n-channel JFET rated with values $I_{DSS} = 10 \text{ mA}$
and $V_p = -3.5 \text{ V}$ is operated with I_D measured
to be 3.265 mA . What is the value of V_{GS} ?

3) The pinch off voltage of FET is -3 V and
drain saturation current is 40 mA . If the gate to
source voltage is -2 V and drain to source
voltage is 4 V . Determine its drain current,
transconductance and DC drain resistance.

2) Bipolar Junction transistor biasing

1) For the given parameters values of voltage
divider biasing circuit, determine the Q-point
of the dc load line and draw the dc load
line. $R_1 = 56 K\Omega$, $R_2 = 10 K\Omega$, $R_C = 2.2 K\Omega$, $R_E = 1 K\Omega$
and $V_{CC} = 12 \text{ V}$.

3) Transistor Amplifiers

1) A 3 stage amplifier has a first stage voltage
gain of 10, second stage voltage gain of 50
and third stage voltage gain of 400. If the
input voltage given at the first stage of
amplifier is $10 \mu\text{V}$. Calculate the output of
each stage. Also find the total voltage gain in
dB

2) Find the voltage gain and input resistance
of a single stage CE Amplifier. If $V_{CC} = 18 \text{ V}$,

$$R_1 = 47k\Omega, R_2 = 12k\Omega, R_C = 3.3k\Omega, R_E = 1000\Omega,$$


$$R_L = 10k\Omega, \beta = 100, V_{BE} = 0.3V, r_e' = 52mV / I_E$$

- 3) For the circuit given below $R_1 = 100k\Omega$,
 $R_2 = 10k\Omega$, $R_C = 2.2k\Omega$, $R_E = 220\Omega$, $V_{CC} = 15V$,
 $I_E = 3.41mA$ and $\beta = 100$, calculate the
 voltage gain, r_e' , power gain, A_V in dB
 and A_P in dB,

- 4) For the CE Amplifier circuit using Silicon transistors
 given below, find

(i) Voltage across $10k\Omega$ (ii) I_E (iii) r_e' (iv) A_V

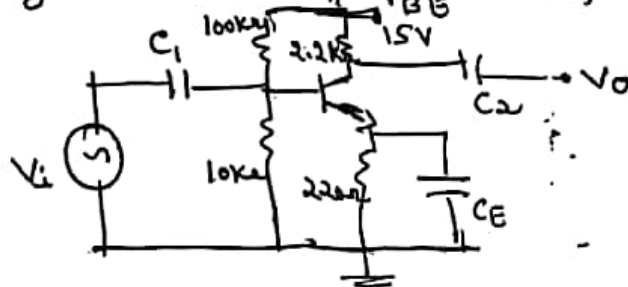(v) A_S . Given $\beta = 100$, $V_{BE} = 0.7V$, $r_e' = \frac{26mV}{I_E}$



- 5) CE Amplifier circuit using Germanium transistors
 is shown in figure, calculate (i) voltage
 across $12k\Omega$ (ii) I_E (iii) $Z_{in}(base)$ (iv) A_V (v) Z_o
 given $r_e' = \frac{52mV}{I_E}$, $V_{BE} = 0.3V$, $\beta = 150$

